

CSE 331 - Computer Organization

Project-3: R-Type and I-Type MIPS

Due date: December 7 Monday-17:00

In this project, you will use Altera Quartus II with Verilog. You will design a part of the 32-bit MIPS processor. The block that you will design will get an 32-bit instruction as its input and compute the resultant value and stores it to the destination register given by the instruction. The **only** supported instructions in your design will be **add, sub, and, or, sra, srl, sll, sltu** and **addi, addiu, andi, ori, slti, lui** instructions. The input of your top-module will be the **instruction only**. The output of your top-module will be the output of your ALU to follow and check its computations during the simulation. You will write the register contents before and after the execution of instructions using **writememh** in your testbench verilog code. You will initialize memory contents using **readmemh**.

R (Register) Format

This divides the instruction into six fields as follows:

| | | | | | |
|-----------|-----------|-----------|-----------|--------------|--------------|
| 6 | 5 | 5 | 5 | 5 | 6 |
| op | rs | rt | rd | shamt | funct |

Where,

op = opcode

rs = identifier of first source register

rt = identifier of second source register

rd = identifier of destination register

shamt = shift amount indicating how many bits the contents of a register must be shifted left or right (only used in shift instructions – NOT used here)

funct = distinguishes among R-type instructions as all R-type instructions have op = 0.

| | | | | |
|--------------|-----------|-----------|-----------|--------------------------|
| BITS: | 31-26 | 25-21 | 20-16 | 15-0 |
| | op | rs | rt | immediate/address |
| | 6 bits | 5 bits | 5 bits | 16 bits |

I-FORMAT INSTRUCTION


op - operation

rs - source register


rt - transition register (made this up)

immediate/address - immediate value

 1. Use behavioral Verilog wherever needed.
2. You will design **Register module** using **behavioral Verilog**. The **register** has **32 registers** each containing **32-bit number**.



3. You will write one **top-level Verilog module** to connect ALU and Register modules accurately to finish the project.
4. You will write a **working testbench** and **simulate your design by ModelSim** as you learnt in the PS.
5. Write testbench and test your design through simulations.
6. The top module should look like this:

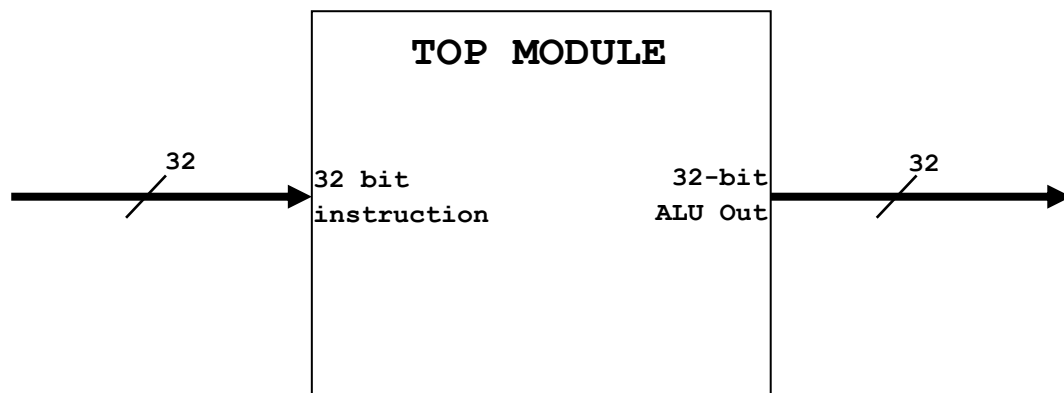

7. Attend the PS to understand the project well and see how you will test the R-type, I-type MIPS on DE0 Board.

Your design should not support J-type or branch instructions. Only the instructions listed above.

Please be sure that your design simulates correctly. Designs that are not even simulating can get at most 20 points.

Submit your Altera Project folder as a zip file to Moodle. We will simulate your design using not only your testbench but also our testbench to see whether all instructions are executing correctly or not.

No late submissions even if it is 1 minute. No medical reports. No excuses. No cry. So start early.

Any cheating attempt with the previous years' projects or with your friends or Internet will result in at least -100 and at most -300. No matter you gave or take the code. Protect your code. Do it yourself for your own good.